

**From:** Huxley Rust  
**Date:** 02/07/2025  
**Subject:** Convolution in Circuit Analysis

## Introduction:

In this lab we set up a circuit and measured the voltages across two capacitors so that we can use convolution and an input response to find out how a circuit will react to a specific input signal.

## Circuit Analysis and Calculations:

	2.2k $\Omega$ resistor	V <sub>o1</sub> Capacitor	V <sub>o2</sub> Capacitor
Expected	2200 $\Omega$	1 $\mu$ F	1 $\mu$ F
Measured	2170.03 $\Omega$	1.04 $\mu$ F	1.04 $\mu$ F
%Error	1.38%	3.85%	3.85%

The s-domain transfer functions that we generated based on the provided circuit in lab were as follows:

$$H_1(s) = \frac{20 \cdot 10^3 (11s + 5000)}{11s^2 + 445 \cdot 10^3 s + 100 \cdot 10^6}$$

$$H_2(s) = \frac{220 \cdot 10^3 s}{11s^2 + 445 \cdot 10^3 s + 100 \cdot 10^6}$$

$H_1(s)$  is the transfer function for  $V_{o1}$  and  $H_2(s)$  is the transfer function  $V_{o2}$ .


## Experimental Procedure and Results:

- **Setup Description:** The function generator configured to output two types of waveforms: a 5 V peak-to-peak square wave with a 2.5 V offset at 10 Hz, and a 5 V peak triangle (sawtooth) wave at 50 Hz with no offset. The circuit was set up as described in the lab 5 material.


- **Waveform Plots:**





[on the next page]



ECE2260 - Lab 5 - Input Signal

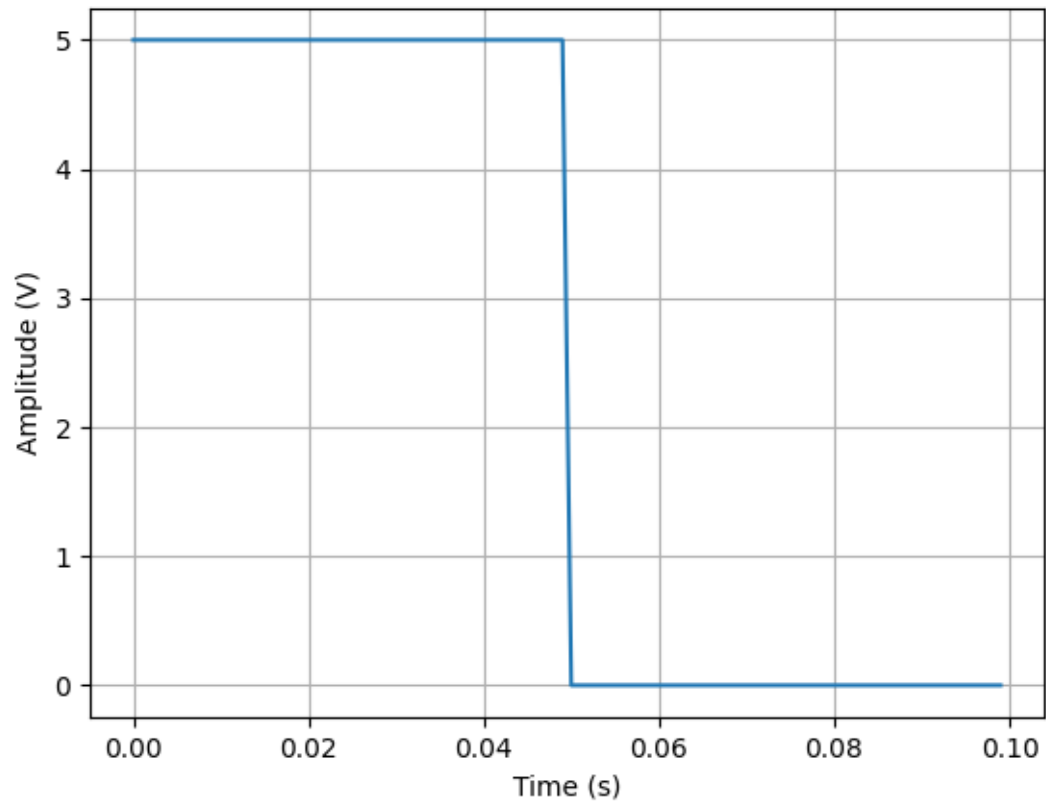


ECE2260 - Lab 5 - Impulse Response

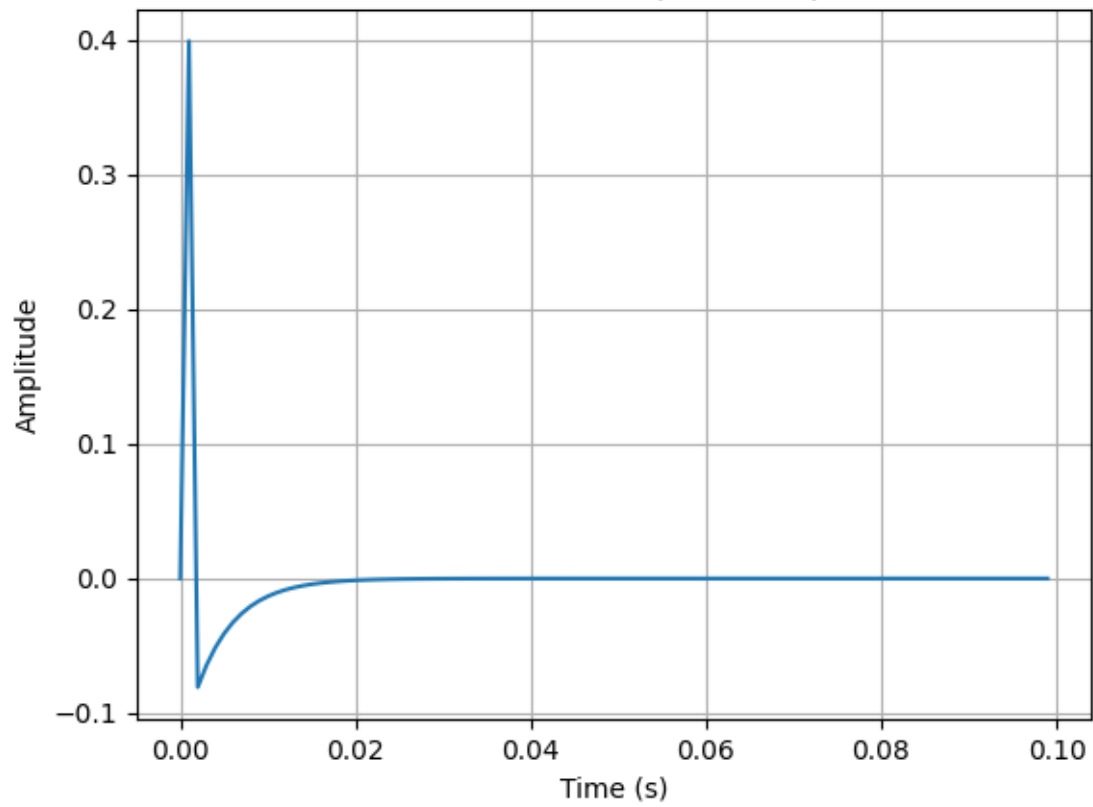

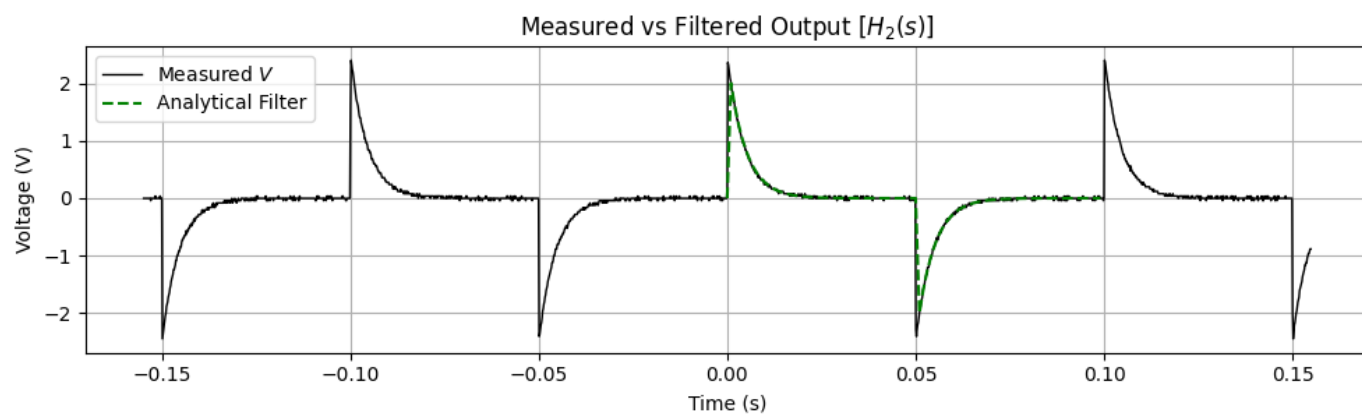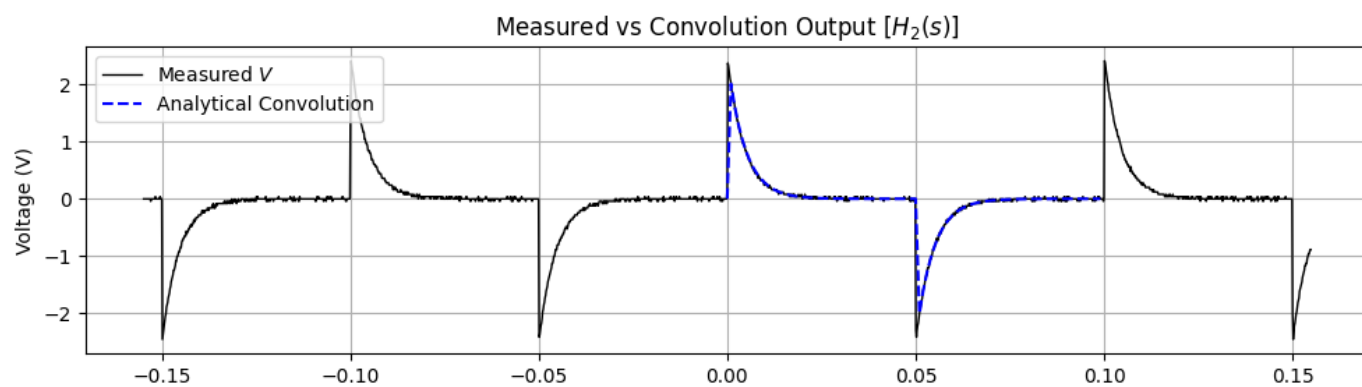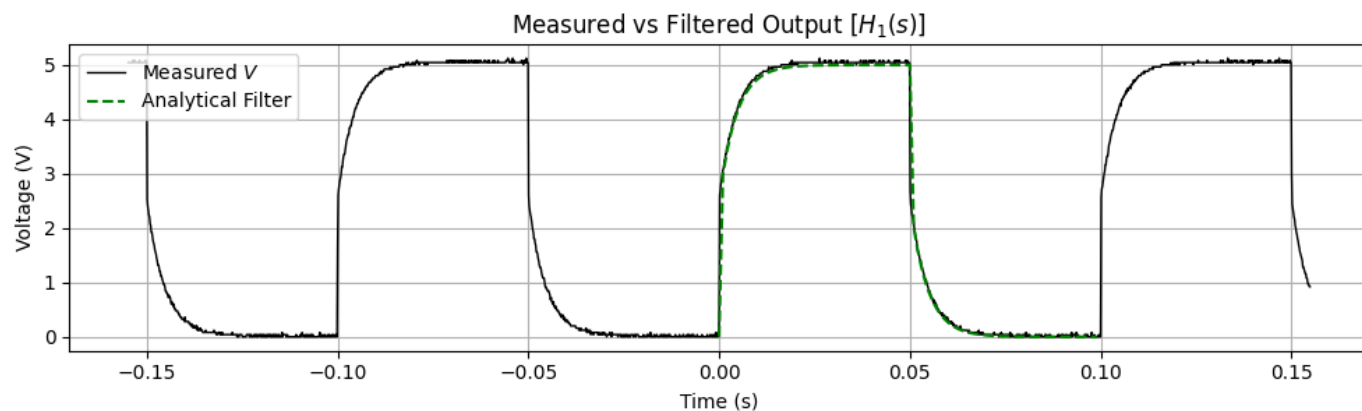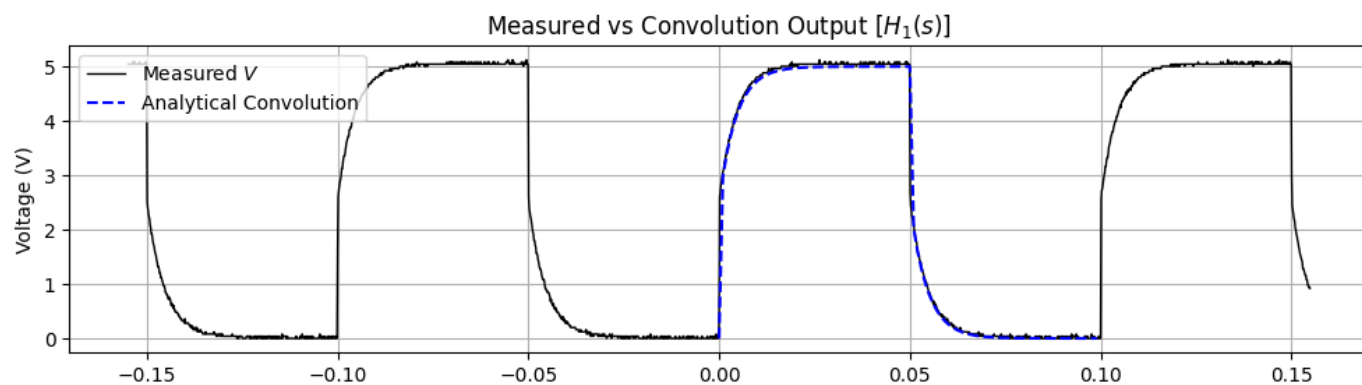

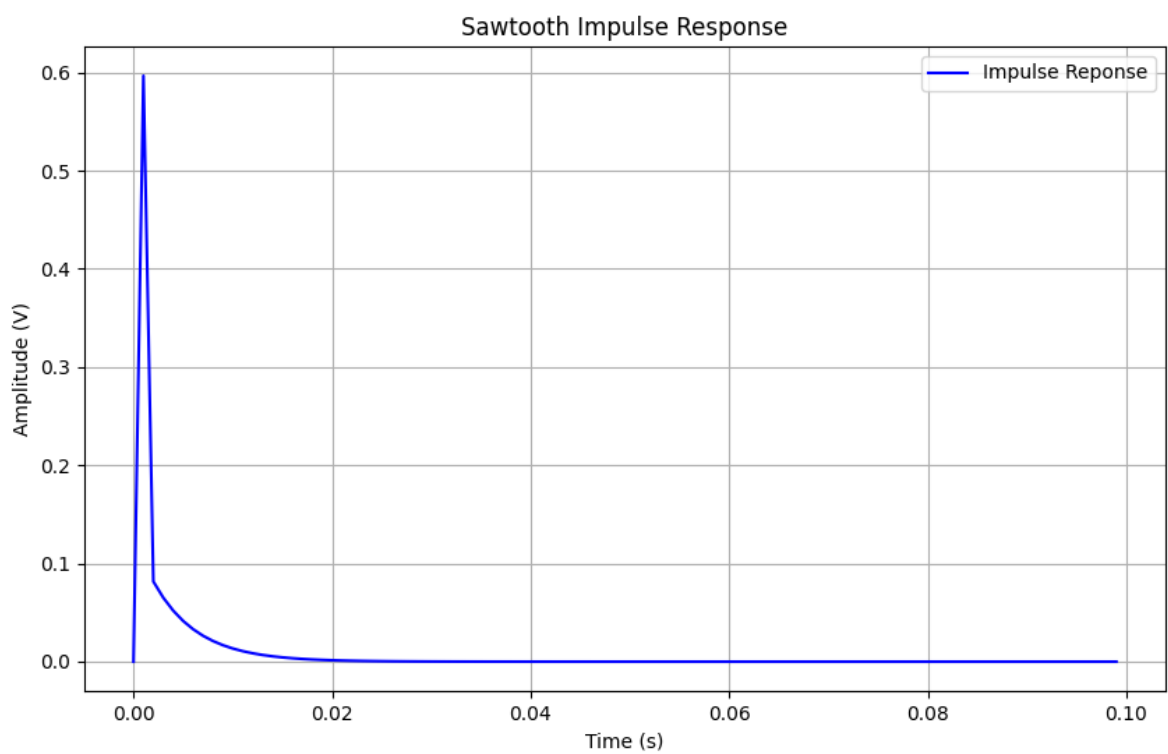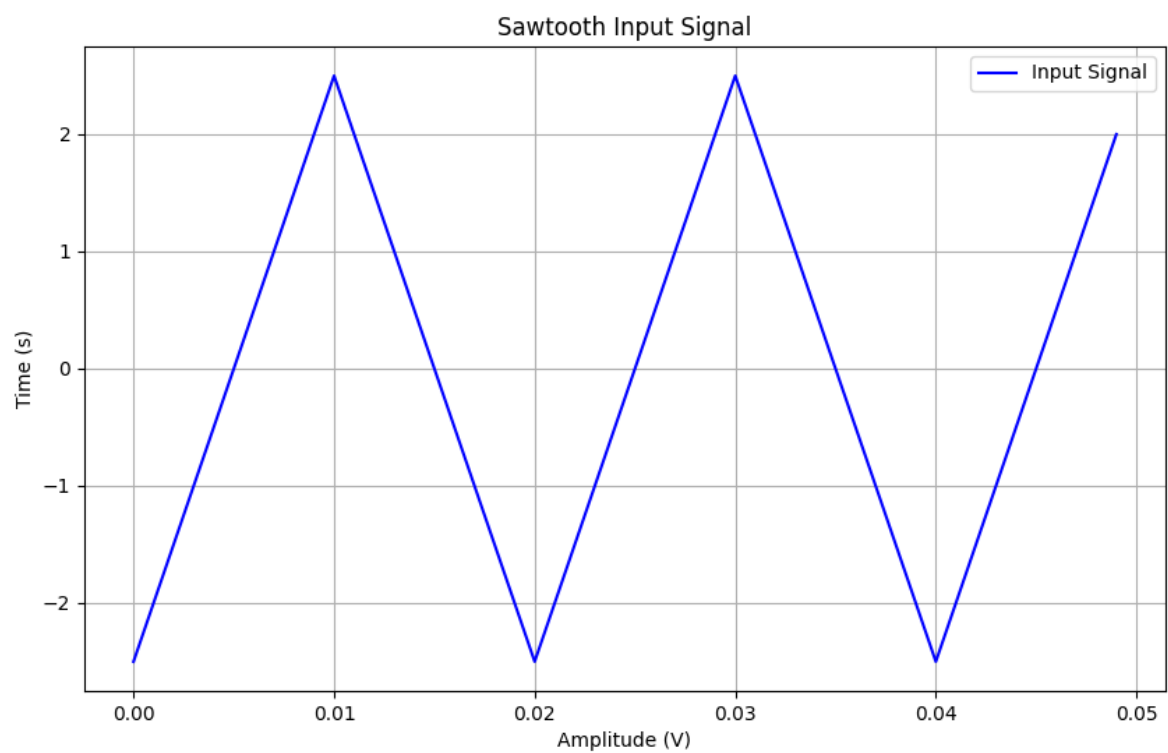

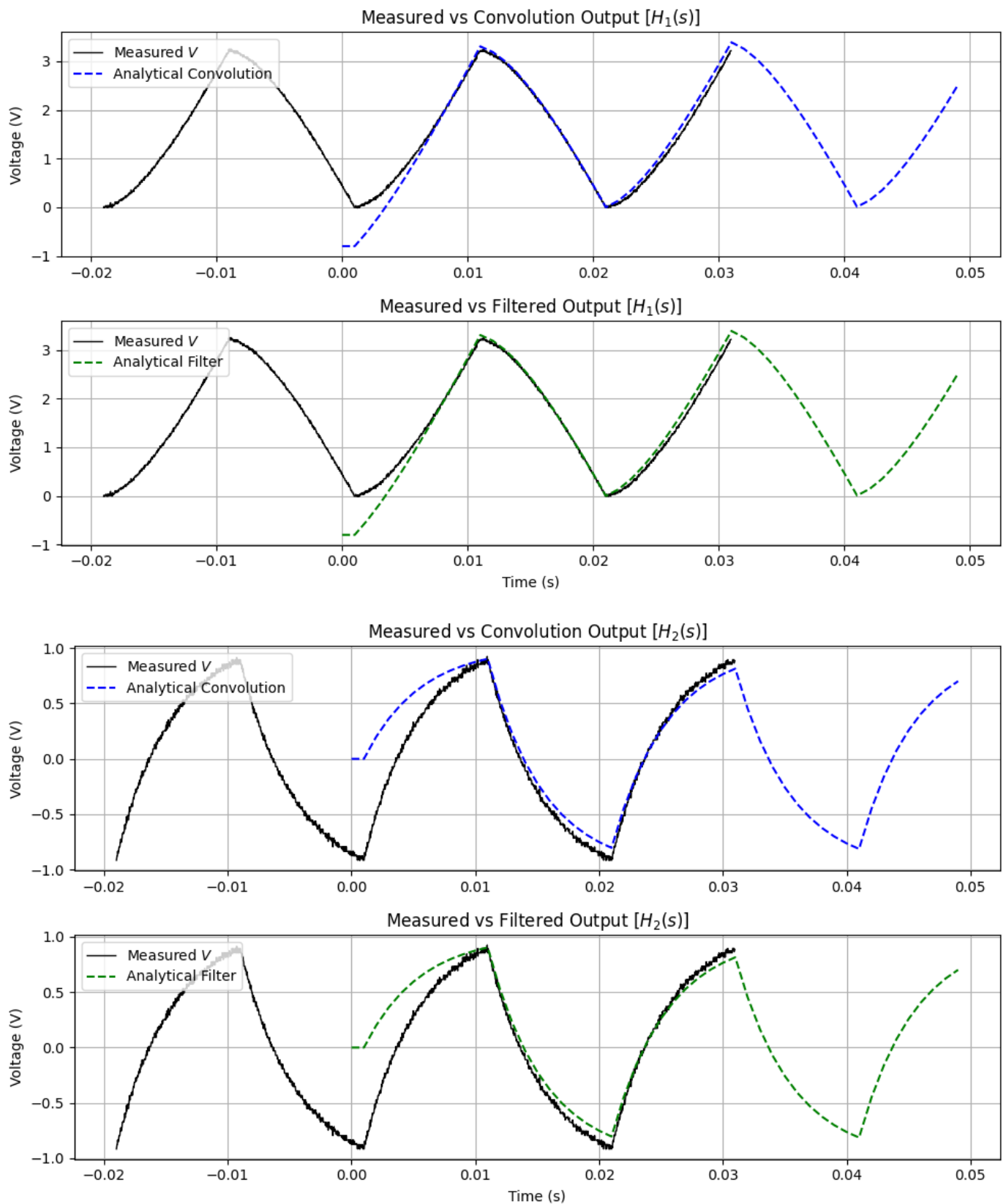

- Quantitative Comparisons:** Our  $H_1(s)$  curve was almost exactly as we had predicted, I was extremely happy with those results. For  $H_2(s)$  I noticed that the peak of the analytical curve wasn't rising nearly as high as the data that we gathered in our measurements. I did change my  $H_2(s)$  equation to include imperfect component values which did help but the analytical graph itself seems to be going from -2 to 2 Volts instead of -2.5 V to 2.5 V. As for the sawtooth waveforms the  $H_1(s)$  prediction was quite close I think maybe the frequency on our oscilloscope was a bit imperfect and drove some odd fluctuations towards the trailing edge of our gathered data. The real interesting part was with  $H_2(s)$  where we saw the analytical data did not rise or trough high or low enough to match the measured data although it was also quite close.

## Conclusion:

In this lab we used convolution and the impulse response to analyze an RC circuit's behavior in the time domain. We derived transfer functions for  $V_{o1}$  and  $V_{o2}$  from the provided circuit in lab 5 material. We applied two different wave forms to the circuit (a 5V square wave and a 5V triangle wave). We used python to model the response using a digital filter and convolution. We then compared the simulated results to the measured data we gathered from the oscilloscopes. While we did see matching data in our  $H_1(S)$  equations we did see some discrepancies in our  $H_2(S)$  equations. If you know the impulse response for a circuit you can use it to find out how a circuit will react to an input signal via convolution.